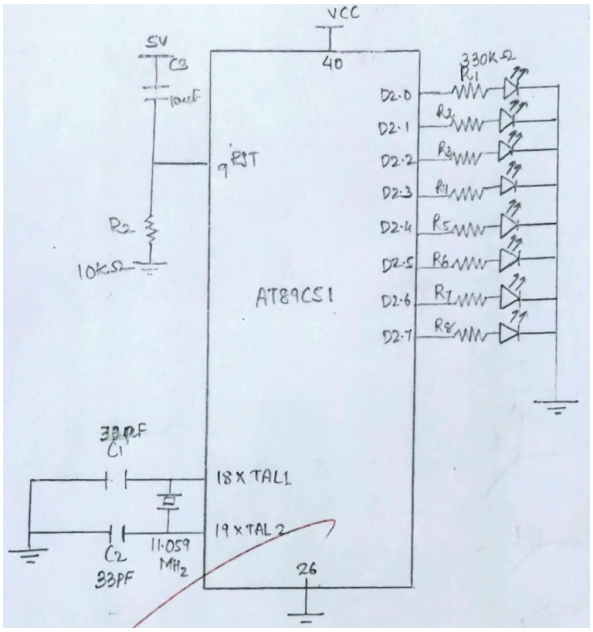
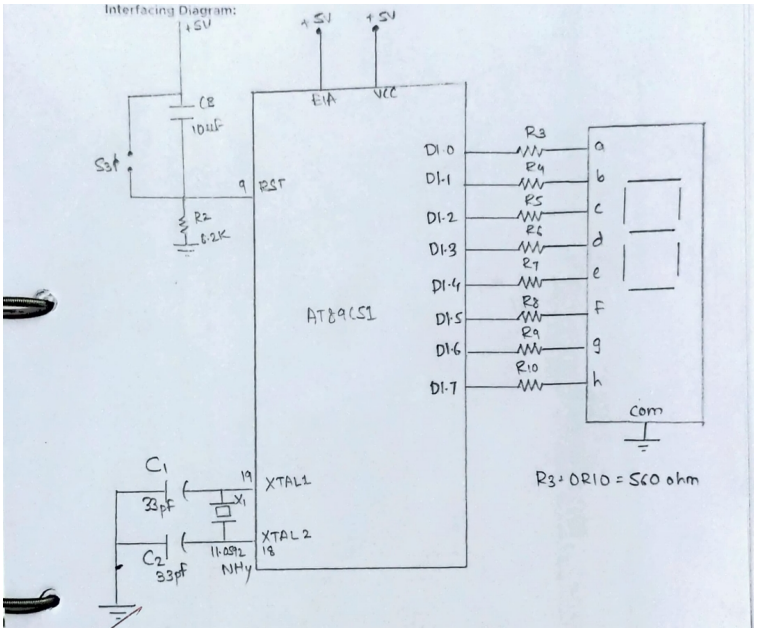
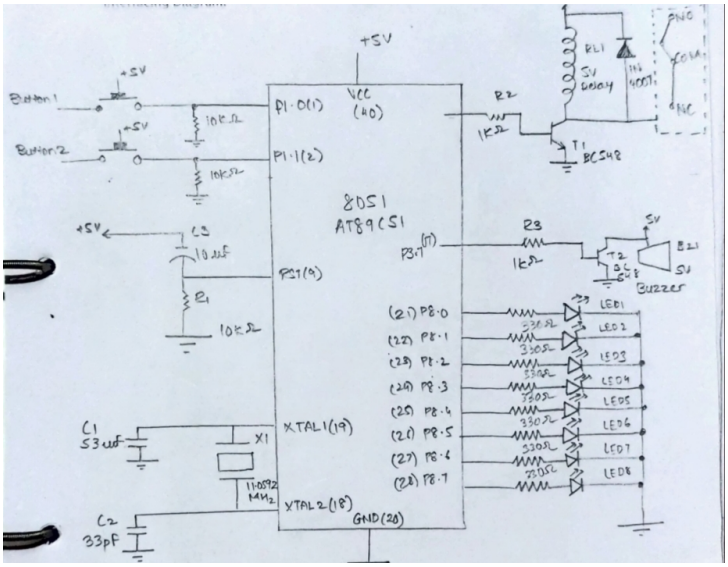
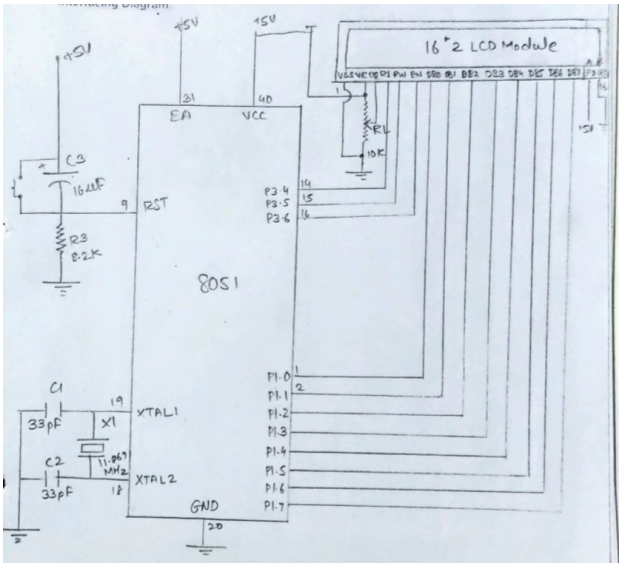
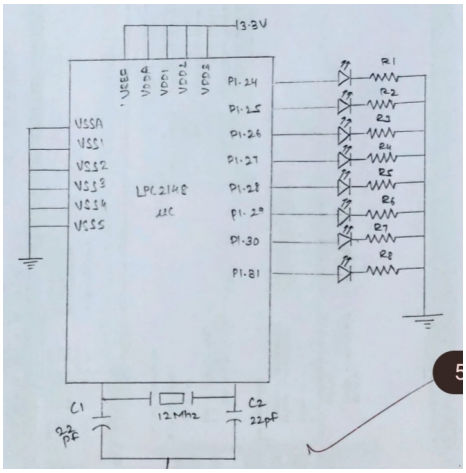
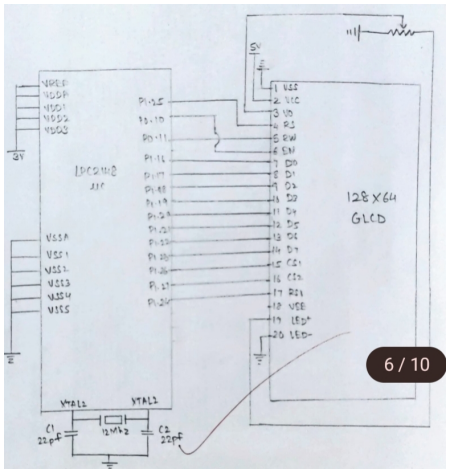

VCC
40
5V
C3
10uF
9 RST
R2
10kΩ
330Ω
D2.0
D2.1
D2.2
D2.3
D2.4
D2.5
D2.6
D2.7
AT89C51
33pF
C1
18 XTAL1
19 XTAL2
C2
33PF
11.059 MHz
26

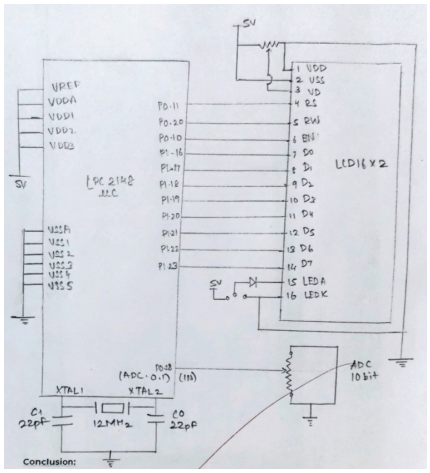

Interfacing Diagram:
+5V
C8
10uF
S3f
9 RST
R2
8.2K
EA
VCC
AT89C51
P1.0
P1.1
P1.2
P1.3
P1.4
P1.5
P1.6
P1.7
R3
R4
R5
R6
R7
R8
R9
R10
a
b
c
d
e
f
g
h
com
C1
33pF
19 XTAL1
X1
XTAL2
18
C2
33pF
11.0592 MHz
R3=OR10=560 ohm

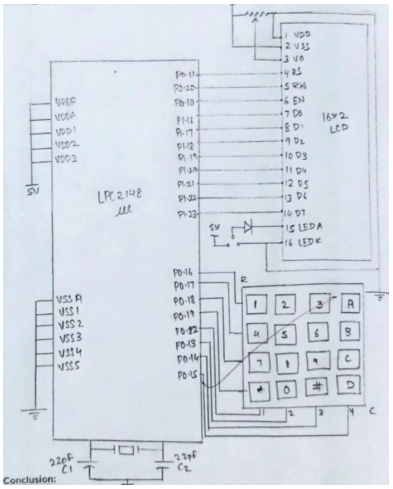

+5V
Button1
Button2
10KΩ
P1.0(1)
P1.1(2)
8051
AT89C51
VCC (40)
R2
1KΩ
RL1
5V Relay
T1
BC548
C3
10 uF
R1
10KΩ
P3.7(11)
R3
1KΩ
T2
BZ1
Buzzer
P3.1(9)
(21) P0.0
(22) P0.1
(23) P0.2
(24) P0.3
(25) P0.4
(26) P0.5
(27) P0.6
(28) P0.7
330Ω
LED1
LED2
LED3
LED4
LED5
LED6
LED7
LED8
C1
33 uF
X1
11.0592 MHz
XTAL1(19)
XTAL2(18)
GND(20)
C2
33pF

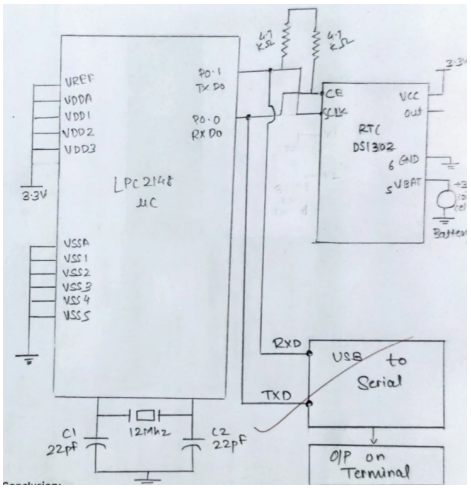

16*2 LCD Module
+5V
EA
VCC
21
40
C3
16uF
9 RST
R3
8.2K
8051
P3.4
P3.5
P3.6
RL
10K
P1.0
P1.1
P1.2
P1.3
P1.4
P1.5
P1.6
P1.7
C1
33pF
19 XTAL1
X1
11.067 MHz
C2
33pF
18 XTAL2
GND
20

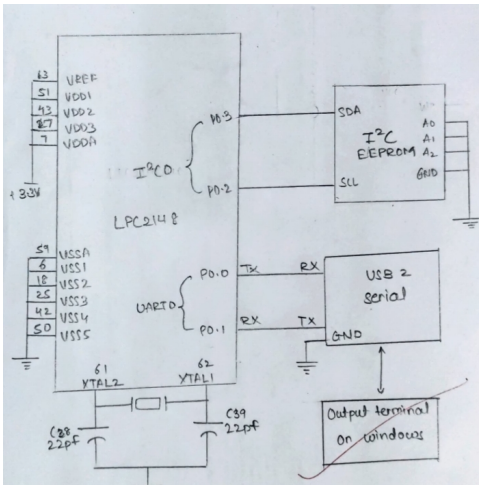

3.3V
VREF
VDDA
VDD1
VDD2
VDD3
P1.24
P1.25
P1.26
P1.27
P1.28
P1.29
P1.30
P1.31
R1
R2
R3
R4
R5
R6
R7
R8
VSSA
VSS1
VSS2
VSS3
VSS4
VSS5
LPC2148
μC
C1
22pF
12MHz
C2
22pF


5V
128X64
GLCD
LPC2148
μC
C1
22pF
12MHz
C2
22pF


5V
LCD16X2
LPC2148
μC
ADC
10 bit
C1
22pF
12MHz
C0
22pF
Conclusion:


16X2
LCD
LPC2148
μC
5V
C1
22pF
12MHz
C2
22pF
Conclusion:


4.7KΩ
4.7KΩ
3.3V
P0.1
TX D0
P0.0
RX D0
LPC2148
μC
RTC
DS1302
CE
SCLK
VCC
GND
VBAT
Battery
RXD
TXD
USB to Serial
O/P on Terminal
C1
22pF
12MHz
C2
22pF


3.3V
LPC2148
I2C
UART0
P0.3
P0.2
P0.0
P0.1
SDA
SCL
I2C EEPROM
A0
A1
A2
GND
TX
RX
USB 2 Serial
GND
Output terminal on windows
C38
22pF
C39
22pF